

# January 2013 Preliminary Exam, Electricity and Magnetism

## Problem 3

Kevin P. Nuckolls (k.nuckolls@princeton.edu)

Solution presented in class by Christian Jepsen

### Problem: Complex Impedances

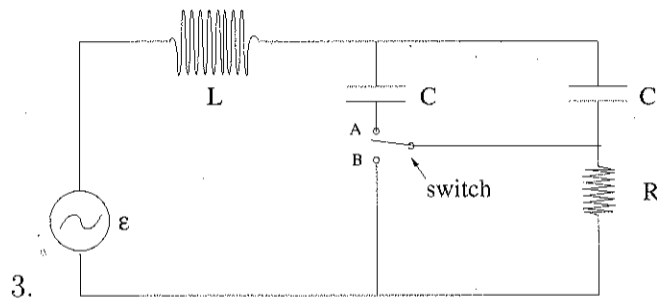


Figure 1: An AC circuit.

Figure 1: Circuit diagram from J13E.3

Consider the circuit above. The switch can be set in any of three positions,  $A$ ,  $B$ , or open (unconnected). The source supplies a voltage  $\epsilon(\omega) = \epsilon_0 e^{i\omega t}$ .

- When the switch is connected to  $A$ , find the frequency  $\omega$  that maximizes the current through the resistor  $R$ .
- If we then flip the switch to the  $B$  position, what is the average power dissipation in the circuit (ignoring transient effects).
- We now open the switch to the middle position. Find the value of the resistor  $R$  that will drop the amplitude of the current to  $1/2$  the value you found in part (a), at the same frequency  $\omega$  you found in part (a).
- Suppose that the inductor, of inductance  $L$ , is constructed from a solenoid with  $N$  turns over a length  $l$ .

Express the cross sectional area of the solenoid in terms of the inductance  $L$ , the number of turns  $N$ , the length  $l$ , and any fundamental constants.

### Solution:

(a) When the switch is flipped to position  $A$ , the equivalent circuit is an LRC circuit, where the two capacitors form an effective capacitance in their parallel configuration of

$$C_{tot} = C + C = 2C \quad (1)$$

We want to consider this voltage, with its complex phase factor, with the system's complex impedances. The complex impedances of a resistor, capacitor, and inductors are  $Z_R = R$ ,  $Z_C = \frac{1}{i\omega C}$ , and  $Z_L = i\omega L$ , respectively. Therefore,

$$\epsilon = IZ_{tot} \quad (2)$$

---


$$\implies |I|^2 = \frac{|\epsilon|^2}{|Z_{tot}|^2} = \frac{\epsilon_0^2}{R^2 + \left(\frac{1}{\omega C_{tot}} - \omega L\right)^2} = \frac{\epsilon_0^2}{R^2 + \left(\frac{1}{2\omega C} - \omega L\right)^2} \quad (3)$$

The current will be maximized for a frequency that makes the second factor in the denominator equal to zero.

$$\frac{1}{2\omega C} = \omega L \quad (4)$$

$$\omega = \sqrt{\frac{1}{2CL}} \quad (5)$$

(b) If the switch is now at position  $B$ , we short the resistor, which reroutes all of the current around it. Thus,  $P = IV = 0$ .

(c) Opening the switch also gives us an LRC circuit, but using only one of the capacitors. We want the value of  $R$  such that the current is half the answer from part (a), using the same frequency as part (a). Therefore,

$$|I_B|^2 = \frac{1}{4}|I_A|^2 = \frac{\epsilon_0^2}{R^2 + \left(\frac{1}{2\omega C} - \omega L\right)^2} = \frac{\epsilon_0^2}{4R^2} \quad (6)$$

$$\implies \left(\frac{1}{2\omega C} - \omega L\right)^2 = 3R^2 \quad (7)$$

$$\implies R = \sqrt{\frac{L}{6C}} \quad (8)$$

(d) The magnetic field in a solenoid of length  $l$  and  $N$  turns is  $B = \mu_0 I \frac{N}{l}$ . By Lenz's law,

$$|\epsilon| = \frac{d\Phi}{dt} = \frac{d}{dt}(B(NA)) = NA \frac{d}{dt} \left( \mu_0 I \frac{N}{l} \right) = \mu_0 \frac{N^2 A}{l} \dot{I} \equiv L \dot{I} \quad (9)$$

$$\implies L = \frac{\mu_0 N^2 A}{l} \implies A = \frac{Ll}{\mu_0 N^2} \quad (10)$$